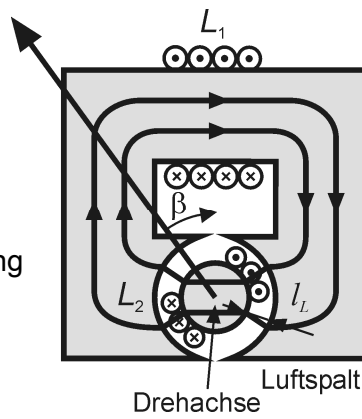


**Aufgabe 1**


1.1 Feldlinien: siehe Abb.

Vorteile:

- $I_L = \text{const}$
  - für alle  $\beta$ :  $B \perp$  Wicklung
- $\Rightarrow$  höheres  $M$



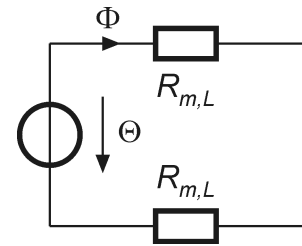1.2  $R_m = 2R_{m,L} = \frac{2l_L}{\mu_0 A_L} = 7,1 \cdot 10^6 \text{ H}^{-1}$



1.3  $\Phi = BA_L = 9 \mu\text{Wb}$       $N_1 = \frac{\Phi_1 R_m}{I_1} = 640$       $L_1 = \frac{N_1^2}{R_{m,L}} = 58 \text{ mH}$

1.4 Stromrichtung: siehe Abb. 1.1

1.5  $F = lBI_2$       $M = N_2 Fd = N_2 lBI_2 d = 1,6 \mu\text{Nm}$

1.6  $M_F = c\beta = M \Rightarrow c = M/\beta_{\text{max}} = 18 \text{ nN/}^\circ$



1.7 Produkt  $I_1 I_2$      Messung von  $P = UI$  an Last  $R$

$L_1$  in Serie zu  $R$  (Strommessung  $I = I_1$ )

$L_2$  mit Serienwiderstand  $R_2 = 10 \text{ k}\Omega$  parallel zur Last  $R$  (Spannungsmessung  $U = R_2 I_2$ )

**Aufgabe 2**

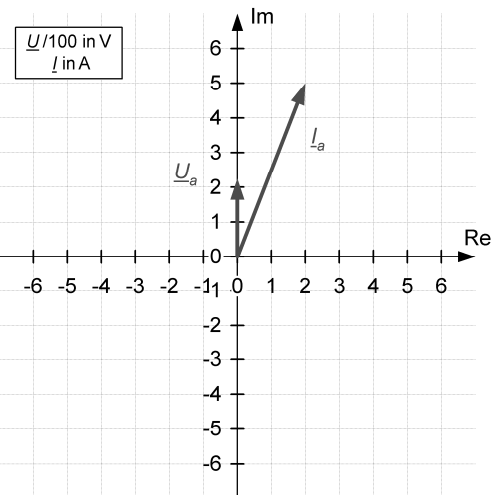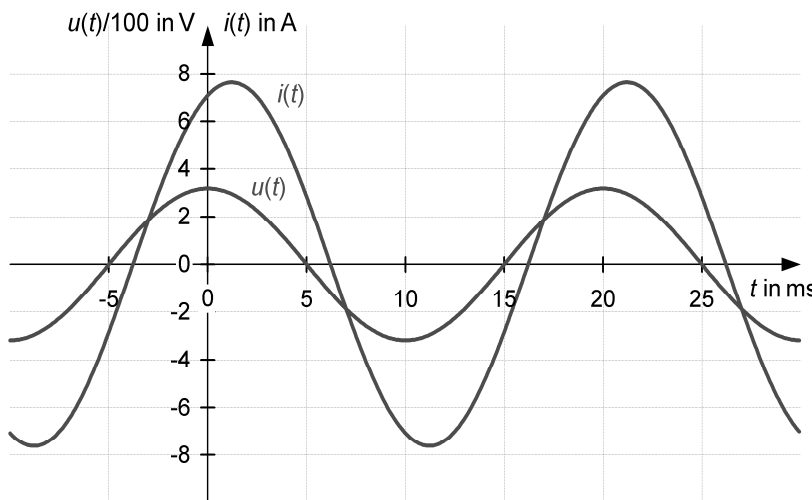2.1  $T = 1/f = 20 \text{ ms}$       $\hat{U}_a = \sqrt{2}U_a = 318 \text{ V}$       $\varphi_u = 90^\circ$



2.2  $\varphi = \text{asin}\beta = 22^\circ$       $\underline{S} = \underline{S}e^{j\varphi} = (1,12 + j0,45) \text{ kVA} = P + jQ \Rightarrow P = 1,12 \text{ kW}, Q = 0,45 \text{ kvar} > 0 \Rightarrow$  induktiv

2.3  $\underline{I}_a^* = \frac{\underline{S}}{\underline{U}_a} = \frac{(1,12 + j0,45) \text{ kVA}}{j225 \text{ V}} = (2 - j5) \text{ A} \Rightarrow \underline{I}_a = (2 + j5) \text{ A}$

2.4  $\underline{Z}_a = \frac{\underline{U}_a}{\underline{I}_a} = \frac{j225 \text{ V}}{(2 + j5) \text{ A}} = (40 + j16) \Omega$       $R$  in Serie mit  $L$       $R_a = 40 \Omega$       $L_a = \frac{X_L}{\omega} = \frac{16 \Omega}{2\pi \cdot 50 \text{ Hz}} = 50 \text{ mH}$

2.5  $\underline{Z}_e = 2\underline{Z}_L + \underline{Z}_C = 2j\omega L + \frac{1}{j\omega C}$       $\underline{H}(f) = \frac{\underline{Z}_C}{\underline{Z}_e} = \frac{1/(j\omega C)}{2j\omega L + 1/(j\omega C)} = \frac{1}{1 - 2\omega^2 LC}$

2.6  $H(f \rightarrow 0) = 1$       $H(f \rightarrow \infty) = 0$      hochfrequente Störungen werden gesperrt


2.7  $L = \frac{1}{2(2\pi f_0)^2 C} = \frac{1}{2(2\pi \cdot 8 \text{ kHz})^2 \cdot 0,1 \mu\text{F}} = 2 \text{ mH}$

### Aufgabe 3

3.1  $R_{iP} = R_1 + R_2 = 8 \Omega$      $U_{0P} = U_1 + R_1 I_1 = 17 \text{ V}$

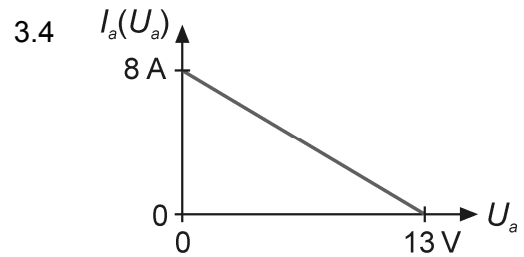3.2  $R_i = R_{iP} \square R_{iB}$      $R_i = \frac{(R_1 + R_2) R_{iB}}{R_1 + R_2 + R_{iB}} = 1,6 \text{ k}\Omega$      $I_P = \frac{U_{0P} - U_{0B}}{R_1 + R_2 + R_{iB}} = \frac{5 \text{ V}}{10 \Omega} = 0,5 \text{ A}$

$U_0 = U_{0B} + R_{iB} I_P = U_{0B} + \frac{R_{iB}(U_{0P} - U_{0B})}{R_1 + R_2 + R_{iB}} = 13 \text{ V}$



3.3  $I_{a,max} = I_k = \frac{U_0}{R_i} = \frac{13 \text{ V}}{1,6 \Omega} = 8,1 \text{ A}$

3.5  $P_{max} = \frac{U_0^2}{4R_i} = \frac{13^2 \text{ V}^2}{6,4 \Omega} = 26,4 \text{ W}$

Wirkungsgrad bei Anpassung nur  $\eta = 0,5 \Rightarrow$  nicht energieeffizient

3.6  $\eta = \frac{P}{P_0} = \frac{R_a}{R_a + R_i} \Rightarrow R_a(1 + \eta^{-1}) = R_i \Rightarrow R_a = R_i \frac{\eta}{1 - \eta}$      $R_{a,min} = \frac{0,95}{1 - 0,95} R_i = 19 \cdot 1,6 \Omega = 30,4 \Omega$

3.7  $P_0 = \frac{U_0^2}{R_a + R_i} = \frac{13^2 \text{ V}^2}{30,4 \Omega + 1,6 \Omega} = 5,3 \text{ W}$      $P = \eta P_0 = 5 \text{ W}$


$I_a = \frac{U_0}{R_a + R_i} = \frac{13 \text{ V}}{30,4 \Omega + 1,6 \Omega} = 0,41 \text{ A}$      $U_a = I_a R_a = 0,41 \text{ A} \cdot 30,4 \Omega = 12,4 \text{ V}$

3.8  $W = Pt = UI t \Rightarrow t_{laden} = \frac{W}{U_0 I_P} = 1,7 \text{ h}$      $t_{entladen} = \frac{W}{U_a I_a} = 2 \text{ h}$

### Aufgabe 4

4.1  $\tau = RC = 1 \text{ ms}$      $I_0 = \frac{U_0}{R} = 2 \text{ mA}$      $u_C(T_0) = U_0(1 - e^{-T_0/\tau}) = 3,5 \text{ V}$

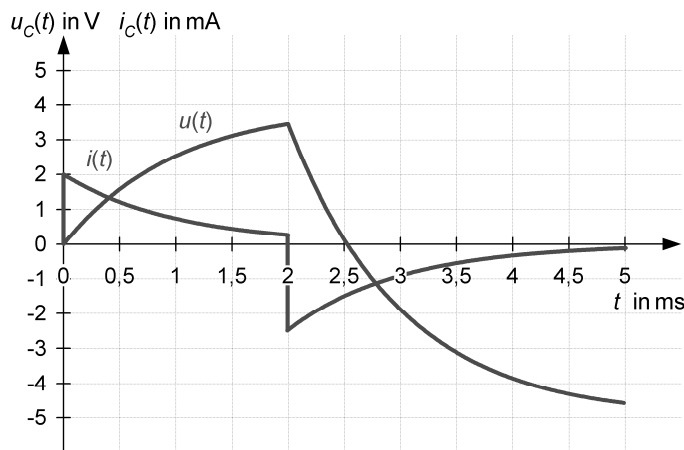4.2  $u_C(t) = U_0(1 - e^{-t/\tau})$      $i_C(t) = I_0 e^{-t/\tau}$




4.3  $u_C(t) = \frac{q(t)}{C} = \frac{I_0 t}{C} = \frac{Uk}{C} t$

$i_C(t) = kU = 0,25 \frac{\text{mA}}{\text{V}} U = \text{const}$

$u_C(T_0) = \frac{U_0 k}{C} T_0 = 2 \frac{\text{V}}{\text{ms}} 2 \text{ ms} = 4 \text{ V}$

$i_C(T_0) = kU_0 = 0,25 \frac{\text{mA}}{\text{V}} 4 \text{ V} = 1 \text{ mA}$

4.4

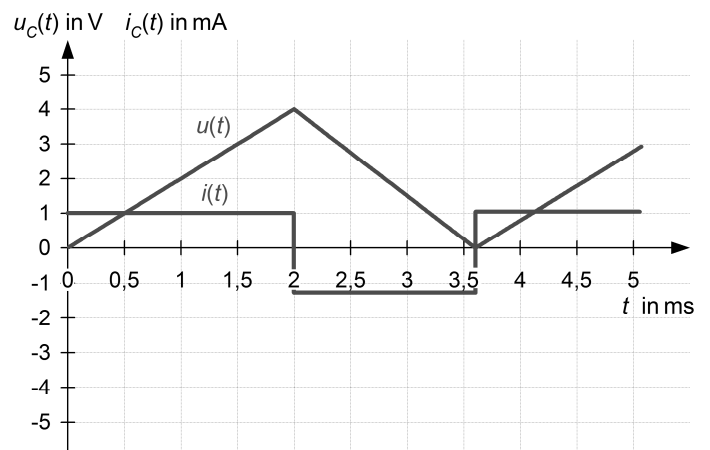


**Aufgabe 1**

- 1.1 im Uhrzeigersinn      1.2  $\Phi = NI = 800 \cdot 0,1 \text{ A} = 80 \text{ A}$
- 1.3  $H = \frac{\theta}{l} = \frac{80 \text{ A}}{0,16 \text{ m}} = 500 \frac{\text{A}}{\text{m}}$       1.4  $B = 0,2 \text{ T}$
- 1.5  $\mu_r = \frac{B}{\mu_0 H} = \frac{0,2 \frac{\text{Vs}}{\text{m}^2}}{4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot 500 \frac{\text{A}}{\text{m}}} = 318$
- 1.6  $R_m = \frac{l}{\mu_0 \mu_r A} = \frac{16 \text{ cm}}{4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot 318 \cdot 1,8 \text{ cm}^2} = 2,2 \cdot 10^6 \text{ H}^{-1}$        $L = \frac{N^2}{R_m} = \frac{800^2}{2,2 \cdot 10^6 \text{ H}^{-1}} = 0,29 \text{ H}$
- 1.7  $\Phi = \frac{\theta}{R_m} = \frac{80 \text{ A}}{2,2 \cdot 10^6 \frac{\text{A}}{\text{Vs}}} = 36 \mu\text{Wb}$        $W = 0,5LI^2 = 0,5 \cdot 0,29 \text{ H} \cdot 0,1^2 \text{ A}^2 = 1,4 \text{ mJ}$
- 1.8  $H = 4 \frac{\text{kA}}{\text{m}}$        $B = 0,6 \text{ T}$

**Aufgabe 2**

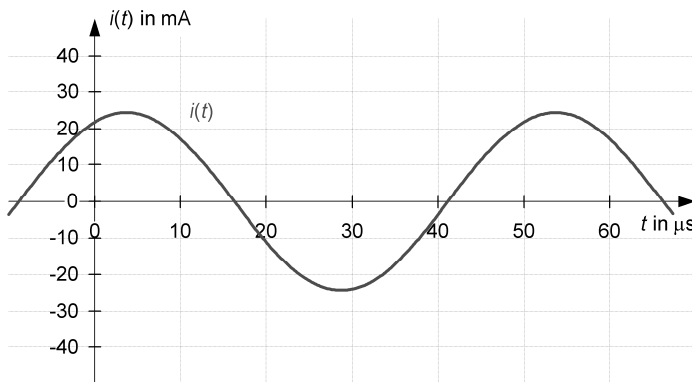- 2.1  $\underline{Z}_R = R = 100 \Omega$        $\underline{Z}_L = j2\pi fL = j125,7 \Omega$        $\underline{Z}_C = \frac{1}{j2\pi fC} = -j79,6 \Omega$
- $\underline{Z} = (\underline{Z}_R + \underline{Z}_L) \parallel \underline{Z}_C = \frac{(100 + j125,7) \Omega \cdot (-j79,6 \Omega)}{(100 + j125,7) \Omega + (-j79,6 \Omega)} = (52,3 - j103,7) \Omega = 116 e^{-j63^\circ} \Omega$
- 2.2  $Z = 116 \Omega$        $\varphi_Z = -63^\circ$
- 2.3  $R = \text{Re}\{\underline{Z}\} = 52,3 \Omega$        $X = \text{Im}\{\underline{Z}\} = -103,7 \Omega$       kapazitiv wegen  $X < 0$
- 2.4  $G = \text{Re}\{\underline{Z}^{-1}\} = 3,9 \text{ mS}$        $B = \text{Im}\{\underline{Z}^{-1}\} = 7,7 \text{ mS}$
- 2.5  $\underline{I} = \frac{U}{\underline{Z}} = \frac{2 \text{ V}}{116 e^{-j63^\circ} \Omega} = 17,2 e^{j63^\circ} \text{ mA} = (7,8 + j15,4) \text{ mA}$
- 2.6  $i(t) = \sqrt{2} \cdot 17,2 \sin(\omega t + 63^\circ) \text{ mA} = 24,3 \sin(2\pi \cdot 20 \text{ kHz} \cdot t + 63^\circ) \text{ mA}$



- 2.7  $\underline{I}_C = \frac{U}{\underline{Z}_C} = \frac{2 \text{ V}}{-j79,6 \Omega} = -j25,1 \text{ mA}$        $\underline{I}_R = \underline{I} - \underline{I}_C = (7,8 + j15,4) \text{ mA} - j25,1 \text{ mA} = (7,8 - j9,7) \text{ mA}$


### Aufgabe 3

3.1  $R_{iV} \rightarrow \infty$

3.2  $U_0 = R_2 I_1 = U_a = 4 \text{ V}$       $R_i = R_2 + R_3 = 20 \text{ k}\Omega$       $I_1 = \frac{U_0}{R_2} = \frac{U_a}{R_2} = \frac{4 \text{ V}}{10 \text{ k}\Omega} = 0,4 \text{ mA}$

3.3  $I_{max} = I_k = \frac{U_0}{R_i} = \frac{4 \text{ V}}{20 \text{ k}\Omega} = 0,2 \text{ mA}$      3.4  $P_{max} = \frac{U_0^2}{4 R_i} = \frac{16 \text{ V}^2}{80 \text{ k}\Omega} = 0,2 \text{ mW}$  für  $R_a = R_i = 20 \text{ k}\Omega$

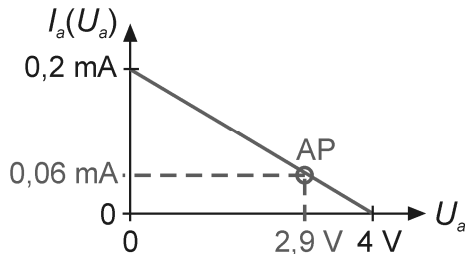3.5  $U_a = U_0 \frac{R_a}{R_a + R_i} = 4 \text{ V} \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 20 \text{ k}\Omega} = 2,9 \text{ V}$   
 $I_a = \frac{U_a}{R_a} = \frac{2,9 \text{ V}}{50 \text{ k}\Omega} = 0,06 \text{ mA}$



3.7  $R_a^* = R_a \parallel R_{iV} = \frac{R_a \cdot R_{iV}}{R_a + R_{iV}} = \frac{50 \text{ k}\Omega \cdot 200 \text{ k}\Omega}{50 \text{ k}\Omega + 200 \text{ k}\Omega} = 40 \text{ k}\Omega$

$U_a^* = U_0 \frac{R_a^*}{R_a^* + R_i} = 4 \text{ V} \frac{40 \text{ k}\Omega}{40 \text{ k}\Omega + 20 \text{ k}\Omega} = 2,7 \text{ V}$

3.8  $f_r = \frac{\Delta U}{U_a} = \frac{-0,2 \text{ V}}{2,9 \text{ V}} = -7 \%$


### Aufgabe 4

4.1  $C_S = \frac{C_1}{8} = 25 \text{ nF}$

4.2  $U_S = 8 U_0 = 560 \text{ kV}$

4.3  $C = \frac{C_S \cdot C_P}{C_S + C_P} = \frac{25 \text{ nF} \cdot 5 \text{ nF}}{25 \text{ nF} + 5 \text{ nF}} = 4,2 \text{ nF}$       $U_L = U_S$  da  $Q_P = 0$  und somit  $U_P = 0$

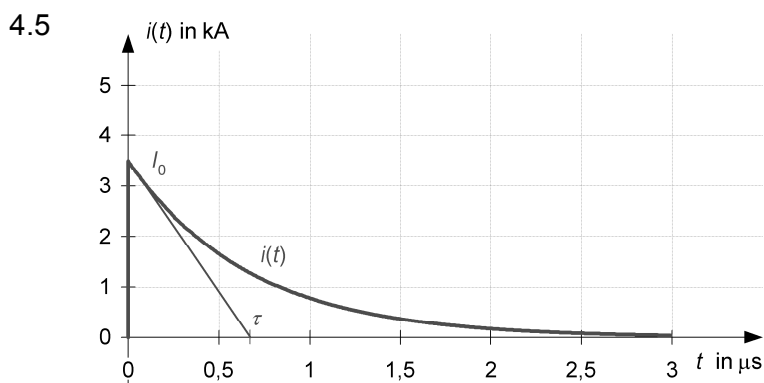4.4  $\tau = RC = 160 \Omega \cdot 4,2 \text{ nF} = 0,67 \mu\text{s}$



$I_0 = \frac{U_L}{R} = \frac{560 \text{ kV}}{160 \Omega} = 3,5 \text{ kA}$

4.6  $Q = C_S U_L = 25 \text{ nF} \cdot 560 \text{ kV} = 14 \text{ mC}$

4.7  $U_S = U_P = \frac{Q}{C_S + C_P} = \frac{14 \text{ mC}}{25 \text{ nF} + 5 \text{ nF}} = 467 \text{ kV}$       $\Delta Q = Q_P = C_P U_P = 5 \text{ nF} \cdot 467 \text{ kV} = 2,3 \text{ mC}$